

# RELATÓRIO- PROJETO 4

## Questão 1


Arquivo exp4ex1.vhd:

```
1  -- *****
2  -- Circuito: Entidade com 3 bits de entrada
3  -- usando 2 multiplexadores 4x1 como componentes
4  --      A  Entrada 1
5  --      B  Entrada 2
6  --      C  Entrada 3
7  --      X  Saída 1 ( $X = (\sim A) \cdot B \cdot C + A \cdot (\sim B) \cdot (\sim C) + A \cdot B$ )
8  --      Y  Saída 2 ( $Y = (\sim A) \cdot (\sim B) + (\sim A) \cdot B \cdot (\sim C) + A \cdot B \cdot C$ )
9  -- *****
10 -----
11 library IEEE;
12 use IEEE.std_logic_1164.all;
13 -----
14
15 entity EXP4EX1 is port (
16     A, B, C :in std_logic;
17     X, Y     :out std_logic);
18 end EXP4EX1;
19
20 architecture ex1 of EXP4EX1 is
21
22     component MULTIPLEXADOR is
23     port (
24         S          :in std_logic_vector (1 DOWNTO 0);
25         D0, D1, D2, D3 :in std_logic;
26         Y          :out std_logic);
27     end component;
28
29     signal not_c : std_logic;
30
31     Begin
32     not_c <= not C;
33     Mux1: MULTIPLEXADOR PORT MAP (D3 => '1', D2 => not_c, D1 => C, D0 => '0', S(1) => A, S(0) => B, Y => X);
34     Mux2: MULTIPLEXADOR PORT MAP (D3 => C, D2 => '0', D1 => not_c, D0 => '1', S(1) => A, S(0) => B, Y => Y);
35 end ex1;
```


## Arquivo tb\_exp4ex1.vhd:

```
12  LIBRARY ieee;
13  USE ieee.std_logic_1164.ALL;
14  USE std.textio.ALL;
15  -----
16
17  ENTITY testbench_exp4ex1 IS END;|
18
19  ARCHITECTURE tb_exp4ex1 OF testbench_exp4ex1 IS
20
21  component EXP4EX1
22
23  port (
24      A, B, C :in  std_logic;
25      X, Y    :out std_logic);
26  end component;
27  -----
28
29  signal aa, bb, cc : std_logic;
30
31  Begin
32
33  mux: EXP4EX1 PORT MAP (A => aa, B => bb, C => cc, X => open, Y => open);
34
35  estimulo: PROCESS
36
37  begin
38
39      aa <= '0'; bb <= '0'; cc <= '0'; wait for 5 ns;
40      cc <= '1'; wait for 5 ns;
41      bb <= '1'; cc <= '0'; wait for 5 ns;
42      cc <= '1'; wait for 5 ns;
43      aa <= '1'; bb <= '0'; cc <= '0'; wait for 5 ns;
44      cc <= '1'; wait for 5 ns;
45      bb <= '1'; cc <= '0'; wait for 5 ns;
46      cc <= '1'; wait for 5 ns;
47
48  end PROCESS estimulo;
49
50  end tb_exp4ex1;
```

## Compilação:

 

## Simulação:

 

|          | Entrada A | Entrada B | Entrada C | Saída X | Saída Y |
|----------|-----------|-----------|-----------|---------|---------|
| Cursor 1 | 0         | 0         | 0         | 0       | 1       |
| Cursor 2 | 0         | 0         | 1         | 0       | 1       |
| Cursor 3 | 0         | 1         | 0         | 0       | 1       |
| Cursor 4 | 0         | 1         | 1         | 1       | 0       |
| Cursor 5 | 1         | 0         | 0         | 1       | 0       |
| Cursor 6 | 1         | 0         | 1         | 0       | 0       |
| Cursor 7 | 1         | 1         | 0         | 1       | 0       |
| Cursor 8 | 1         | 1         | 1         | 1       | 1       |

## Questão 2

Arquivo exp4ex2.vhd:

```
1  -- *****
2  -- Circuito: Entidade com 7 bits de entrada
3  -- usando 1 multiplexador 8x1 e um
4  -- decodificador 4x16 como componentes
5  -- A, B, C e D serão as entradas do decodificador
6  -- e E, F e G atuarão como seletores para o multiplexador
7  --     A Entrada 1 (Bit mais significativo)
8  --     B Entrada 2
9  --     C Entrada 3
10 --     D Entrada 4
11 --     E Seletor 1 (Bit mais significativo)
12 --     F Seletor 2
13 --     G Seletor 3
14 --     S Saída
15 --     S = (F·G + A·B·C·D·(¬E)·(¬F)·G +
16 --         (¬A)·(¬B)·(¬C)·(¬D)·(¬E)·(¬F)·G +
17 --         A·(¬B)·C·E·F·(¬G) + (¬A)·B·C·D·(¬E)·F·(¬G) +
18 --         A·B·C·D·E·(¬F)·(¬G) + A·(¬B)·(¬C)·D·E·(¬F)·(¬G))
19 -- *****

20 -----
21 library IEEE;
22 use IEEE.std_logic_1164.all;
23 -----
24
25 entity EXP4EX2 is port (
26     A, B, C, D, E, F, G :in std_logic;
27     S :out std_logic);
28 end EXP4EX2;
29
30 architecture ex2 of EXP4EX2 is
31
32     component DECODIFICADOR4X16 is
33     port (
34         A :in std_logic_vector (3 DOWNTO 0);
35         Y :out std_logic_vector (15 DOWNTO 0));
36     end component;
37
38     component MULTIPLEXADOR8X1 is
39     port (
40         D :in std_logic_vector (7 DOWNTO 0);
41         S :in std_logic_vector (2 DOWNTO 0);
42         Y :out std_logic);
43     end component;
44
45     signal Y_signal : std_logic_vector (15 DOWNTO 0);
46     signal D_signal : std_logic_vector (7 DOWNTO 0);
47     signal Y015, Y915, Y1011 : std_logic;
48
49     Begin
50     dec: DECODIFICADOR4X16 PORT MAP (A(3) => A, A(2) => B, A(1) => C, A(0) => D, Y => Y_signal);
51
52     Y015 <= Y_signal(0) or Y_signal(15);
53     Y915 <= Y_signal(9) or Y_signal(15);
54     Y1011 <= Y_signal(10) or Y_signal(11);
55
56     D_signal(0) <= '0';
57     D_signal(1) <= Y015;
58     D_signal(2) <= '0';
59     D_signal(3) <= '1';
60     D_signal(4) <= Y915;
61     D_signal(5) <= '0';
62     D_signal(6) <= Y1011;
63     D_signal(7) <= '1';
64
65     mux: MULTIPLEXADOR8X1 PORT MAP (D => D_signal, S(2) => E, S(1) => F, S(0) => G, Y => S);
66 end ex2;
```

## Arquivo tb\_exp4ex2.vhd:

```
21 -----
22 LIBRARY ieee;
23 USE ieee.std_logic_1164.ALL;
24 USE std.textio.ALL;
25 USE ieee.numeric_std.ALL;
26 -----
27
28 ENTITY testbench_exp4ex2 IS END;
29
30 ARCHITECTURE tb_exp4ex2 OF testbench_exp4ex2 IS
31
32     component EXP4EX2
33
34     port (
35         A, B, C, D, E, F, G :in  std_logic;
36         S                    :out std_logic);
37     end component;
38     -----
39
40     signal entrada : std_logic_vector (6 DOWNTO 0);
41
42     Begin
43
44     mux: EXP4EX2 PORT MAP (E => entrada(6), F => entrada(5), G => entrada(4), A => entrada(3), B => entrada(2), C => entrada(1), D => entrada(0), S => open);
45
46     estimulo: PROCESS
47
48     begin
49         for i in 0 to 127 loop
50             entrada <= std_logic_vector(to_unsigned(i, 7));
51             wait for 5 ns;
52         end loop;
53     end PROCESS estimulo;
54
55     end tb_exp4ex2;
```

## Compilação:



| Name                  | Status | Type | Or | Modified               |
|-----------------------|--------|------|----|------------------------|
| exp4ex2.vhd           | ✓      | VHDL | 0  | 03/12/2021 09:23:25 pm |
| multiplexador8x1.v... | ✓      | VHDL | 1  | 03/05/2021 04:25:31 pm |
| tb_exp4ex2.vhd        | ✓      | VHDL | 2  | 03/12/2021 09:22:54 pm |
| decodificador4x16.... | ✓      | VHDL | 3  | 03/05/2021 05:27:17 pm |

Project x sim x

Transcript

```
# Compile of exp4ex2.vhd was successful.
# Compile of multiplexador8x1.vhd was successful.
# Compile of tb_exp4ex2.vhd was successful.
# Compile of decodificador4x16.vhd was successful.
# 4 compiles, 0 failed with no errors.
```

## Simulação:

  

|          | Seletor E | Seletor F | Seletor G | Entrada A | Entrada B | Entrada C | Entrada D | Saída S |
|----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|---------|
| Cursor 1 | 0         | 0         | 0         | 1         | 1         | 1         | 1         | 0       |
| Cursor 2 | 0         | 0         | 1         | 0         | 0         | 0         | 0         | 1       |
| Cursor 3 | 0         | 1         | 0         | 1         | 1         | 1         | 1         | 0       |
| Cursor 4 | 0         | 1         | 1         | 0         | 0         | 0         | 0         | 1       |
| Cursor 5 | 1         | 0         | 0         | 1         | 0         | 0         | 1         | 1       |
| Cursor 6 | 1         | 0         | 1         | 1         | 1         | 1         | 1         | 0       |
| Cursor 7 | 1         | 1         | 0         | 1         | 0         | 1         | 1         | 1       |
| Cursor 8 | 1         | 1         | 1         | 0         | 0         | 0         | 0         | 1       |