

RELATÓRIO- PROJETO 3

Questão 1


Arquivo multiplexador8x1.vhd:

```
1  -- *****
2  --  Circuito: Multiplexador 8x1
3  --          D   Vetor de Entradas
4  --          S   Seletor
5  --          Y   Saída
6  -- *****
7  -----
8  library IEEE;
9  use IEEE.std_logic_1164.all;
10 -----
11
12 entity MULTIPLEXADOR8X1 is port (
13     D :in std_logic_vector (7 DOWNTO 0);
14     S :in std_logic_vector (2 DOWNTO 0);
15     Y :out std_logic);
16 end MULTIPLEXADOR8X1;
17 -----
18
19 architecture mux8x1 of MULTIPLEXADOR8X1 is
20 begin
21
22     Y <= D(0) when S = "000" else
23         D(1) when S = "001" else
24         D(2) when S = "010" else
25         D(3) when S = "011" else
26         D(4) when S = "100" else
27         D(5) when S = "101" else
28         D(6) when S = "110" else
29         D(7) when S = "111";
30 end mux8x1;
```


Arquivo tb_multiplexador8x1.vhd:


```
7
8  ENTITY testbench_mux8x1 IS END;
9
10 -----
11  LIBRARY ieee;
12  USE ieee.std_logic_1164.ALL;
13  USE std.textio.ALL;
14  USE ieee.numeric_std.ALL;
15  -----
16
17  ARCHITECTURE tb_multiplexador8x1 OF testbench_mux8x1 IS
18
19      component MULTIPLEXADOR8X1
20
21      port(
22          S :in std_logic_vector (2 DOWNTO 0);
23          D :in std_logic_vector (7 DOWNTO 0);
24          Y :out std_logic);
25      end component;
26  -----
27
28  signal clk  : std_logic_vector (7 DOWNTO 0);
29  signal tb_s : std_logic_vector (2 DOWNTO 0);
30
31  Begin
32
33  mux: MULTIPLEXADOR8X1 PORT MAP (D => clk, S => tb_s, Y => open);
34
35
36  --Implementacao do processo de estimulo
37
38  clock: PROCESS
39  begin
40      for i in 0 to 255 loop
41          clk <= std_logic_vector(to_unsigned(i, 8));
42          wait for 1 ns;
43      end loop;
44  end process;
45
46
47  tbs: PROCESS
48  begin
49      tb_s <= "000" , "001" after 256 ns, "010" after 512 ns, "011" after 768 ns,
50          "100" after 1024 ns, "101" after 1280 ns, "110" after 1536 ns, "111" after 1792 ns;
51          wait for 2048 ns;
52  end PROCESS;
53
54  end tb_multiplexador8x1;
```

Compilação:

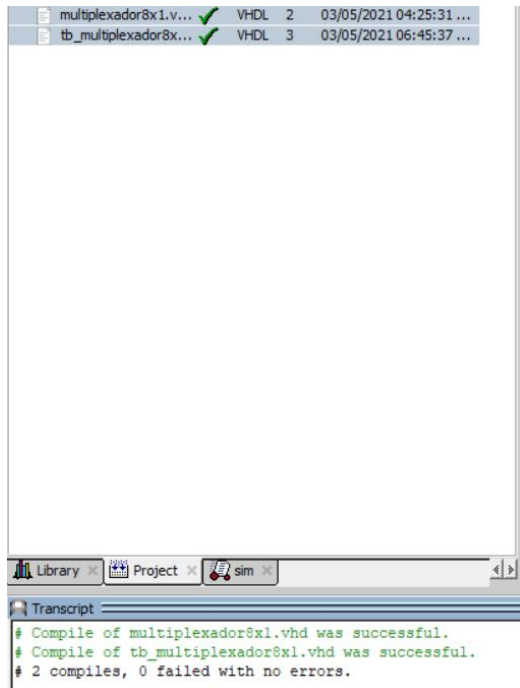

Simulação:

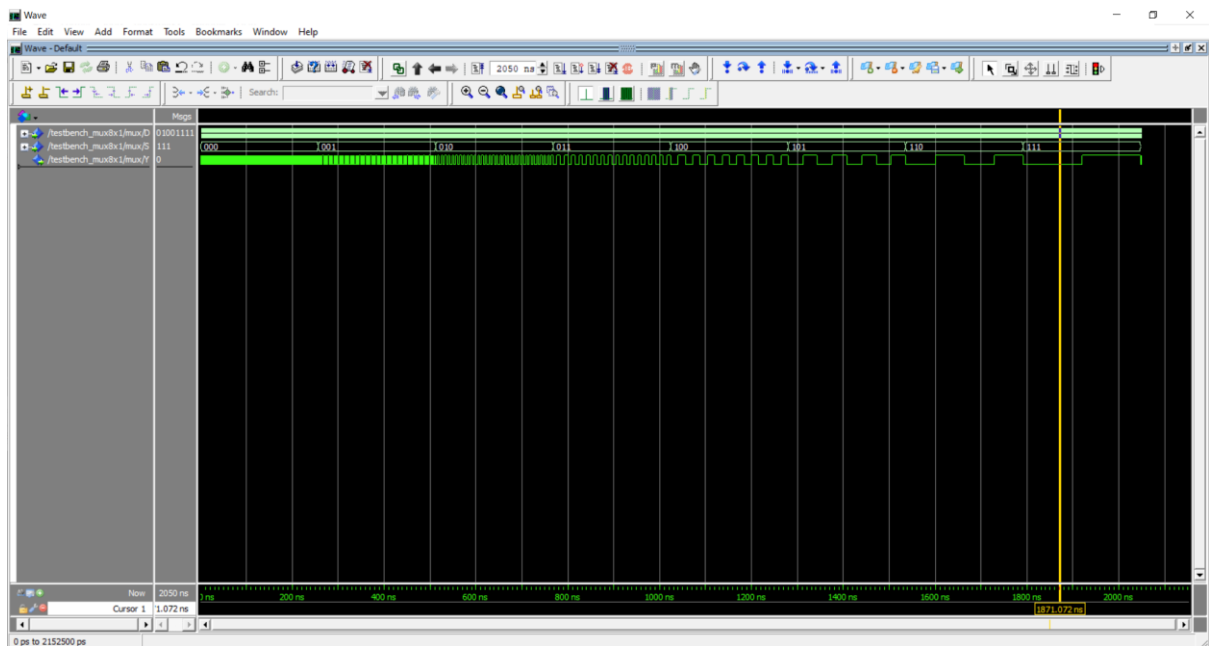

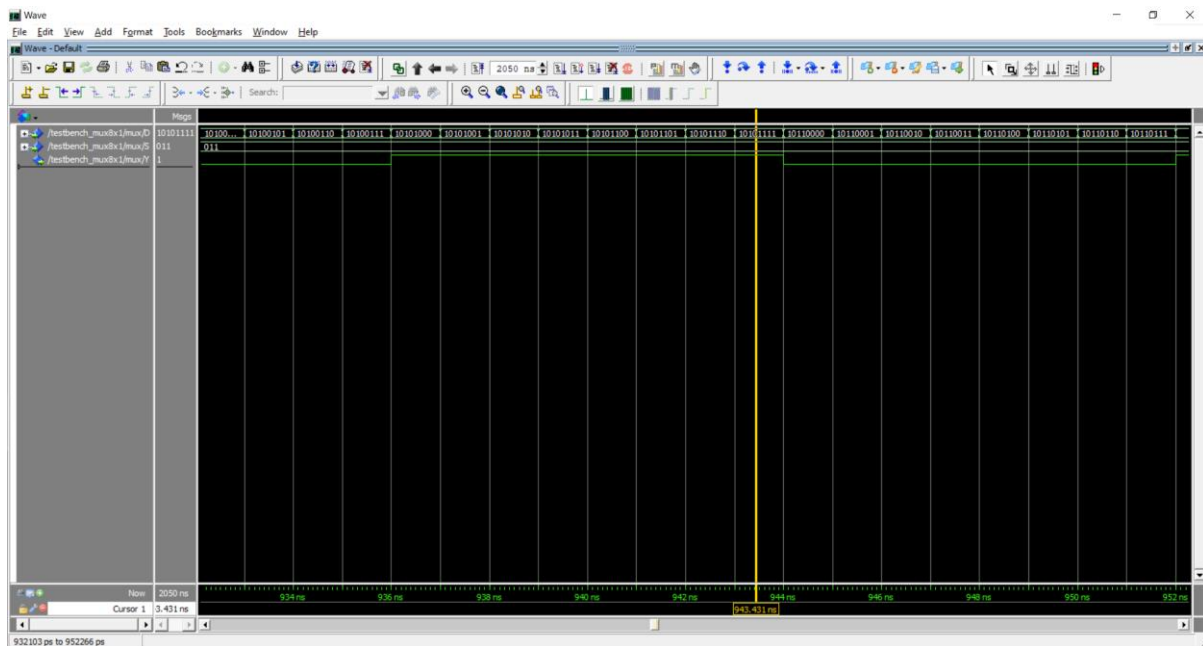

Questão 2

Arquivo decodificador4x16.vhd:

```

6  -----
7  library IEEE;
8  use IEEE.std_logic_1164.all;
9  -----
10
11 entity DECODIFICADOR4X16 is port (
12     A :in  std_logic_vector (3  DOWNT0 0);
13     Y :out std_logic_vector (15 DOWNT0 0));
14 end DECODIFICADOR4X16;
15 -----
16
17 architecture dec4x16 of DECODIFICADOR4X16 is
18 begin
19     with A select
20     Y <= "0000000000000001" when "0000",
21         "0000000000000010" when "0001",
22         "0000000000000100" when "0010",
23         "0000000000001000" when "0011",
24         "0000000000010000" when "0100",
25         "0000000000100000" when "0101",
26         "0000000001000000" when "0110",
27         "0000000010000000" when "0111",
28         "0000000100000000" when "1000",
29         "0000001000000000" when "1001",
30         "0000010000000000" when "1010",
31         "0000100000000000" when "1011",
32         "0001000000000000" when "1100",
33         "0010000000000000" when "1101",
34         "0100000000000000" when "1110",
35         "1000000000000000" when "1111",
36         "0000000000000000" when others;
37 end dec4x16;

```

Arquivo tb_decodificador4x16.vhd:

```
7  ENTITY testbench_dec4x16 IS END;
8
9  -----
10 LIBRARY ieee;
11 USE ieee.std_logic_1164.ALL;
12 USE std.textio.ALL;
13 use ieee.std_logic_signed.ALL;
14 -----
15
16 ARCHITECTURE tb_decodificador4x16 OF testbench_dec4x16 IS
17
18     component DECODIFICADOR4X16
19
20     port(
21         A :in  std_logic_vector (3  DOWNT0 0);
22         Y :out std_logic_vector (15 DOWNT0 0));
23     end component;
24     -----
25
26     signal A : std_logic_vector (3  DOWNT0 0);
27     signal Y : std_logic_vector (15 DOWNT0 0);
28
29     Begin
30
31     dec: DECODIFICADOR4x16 PORT MAP (A => A, Y => Y);
32
33     --Implementacao do processo de estimulo
34
35     A <= "0000"           , "0001" after 5  ns, "0010" after 10 ns, "0011" after 15 ns,
36         "0100" after 20 ns, "0101" after 25 ns, "0110" after 30 ns, "0111" after 35 ns,
37         "1000" after 40 ns, "1001" after 45 ns, "1010" after 50 ns, "1011" after 55 ns,
38         "1100" after 60 ns, "1101" after 65 ns, "1110" after 70 ns, "1111" after 75 ns;
39
40     end tb_decodificador4x16;
```

Compilação:

Project - C:/Users/david/Documents/UnB/2020.2/LSD/projeto 3/projeto3

Name	Status	Type	Order	Modified
tb_decodificador4x16...	✓	VHDL	1	03/05/2021 05:25:06 ...
decodificador4x16...	✓	VHDL	0	03/05/2021 05:27:17 ...

Library Project

Transcript

```
# Compile of decodificador4x16.vhd was successful.  
# Compile of tb_decodificador4x16.vhd was successful.  
# 2 compiles, 0 failed with no errors.
```

ModelSim>

Simulação:

