

RELATÓRIO- PROJETO 5

Questão 1


Arquivo exp5_ex1.vhd:

```
1  -- *****
2  {-- Circuito: Somador de 4 palavras
3  -- usando 4 somadores completos
4  -- ..... A,B ..... Vetores de Entrada
5  -- ..... S ..... Vetor de Saída
6  -- *****
7  -----
8  library IEEE;
9  use IEEE.std_logic_1164.all;
10 -----
11 entity EXP5_EX1 is port (
12     A, B :in  std_logic_vector(3 DOWNTO 0);
13     S     :out std_logic_vector(4 DOWNTO 0));
14 end EXP5_EX1;
15 -----
16
17 architecture ex1 of EXP5_EX1 is
18
19     component SOMADOR_COMPLETO is
20     port (
21         A      :in std_logic;
22         B      :in std_logic;
23         Cin    :in std_logic;
24         S      :out std_logic;
25         Cout   :out std_logic );
26     end component;
27
28     signal Cout_aux : std_logic_vector(2 DOWNTO 0);
29
30 begin
31     som1: SOMADOR_COMPLETO PORT MAP (Cin => '0', A => A(0), B => B(0), S => S(0), Cout => Cout_aux(0));
32     som2: SOMADOR_COMPLETO PORT MAP (Cin => Cout_aux(0), A => A(1), B => B(1), S => S(1), Cout => Cout_aux(1));
33     som3: SOMADOR_COMPLETO PORT MAP (Cin => Cout_aux(1), A => A(2), B => B(2), S => S(2), Cout => Cout_aux(2));
34     som4: SOMADOR_COMPLETO PORT MAP (Cin => Cout_aux(2), A => A(3), B => B(3), S => S(3), Cout => S(4));
35 end ex1;
```




Arquivo tb_exp5_ex1.vhd:

```
9  LIBRARY ieee;
10 USE ieee.std_logic_1164.ALL;
11 USE std.textio.ALL;
12 USE ieee.numeric_std.ALL;
13 -----
14
15 ENTITY testbench_exp5_ex1 IS END;
16
17 ARCHITECTURE tb_exp5_ex1 OF testbench_exp5_ex1 IS
18
19   component EXP5_EX1
20
21   port (
22     A, B :in  std_logic_vector(3 DOWNTO 0);
23     S    :out std_logic_vector(4 DOWNTO 0));
24   end component;
25   -----
26
27   signal aa, bb : std_logic_vector (3 DOWNTO 0);
28
29   Begin
30
31   som: EXP5_EX1 PORT MAP (A => aa, B => bb, S => open);
32
33   estimulo: PROCESS
34
35   begin
36     for i in 0 to 15 loop
37       aa <= std_logic_vector(to_unsigned(i, 4));
38       for j in 0 to 15 loop
39         bb <= std_logic_vector(to_unsigned(j, 4));
40         wait for 5 ns;
41       end loop;
42     end loop;
43   end PROCESS estimulo;
44
45   end tb_exp5_ex1;
```

Compilação:

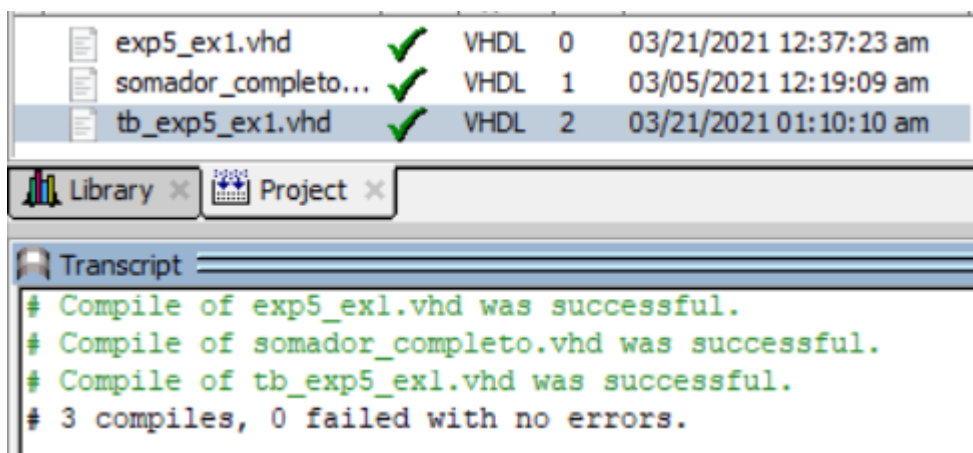

Simulação:

   

	Entrada A	Entrada B	Saída S
Cursor 1	0000	1101	01101
Cursor 2	0001	1000	01001
Cursor 3	0010	0011	00101
Cursor 4	0111	1011	10010
Cursor 5	1000	1000	10000
Cursor 6	1001	0010	01011
Cursor 7	1110	0101	10011
Cursor 8	1111	1111	11110

Questão 2

Arquivo exp5ex2.vhd:

```
1  -- *****
2  -- Circuito: Somador de 4 palavras usando o
3  -- operador '+' da biblioteca std_logic_arith
4  --           A,B   Vetores de Entrada
5  --           S     Vetor de Saída
6  -- *****
7  -----
8  library IEEE;
9  use IEEE.std_logic_1164.all;
10 use IEEE.std_logic_arith.all;
11 -----
12 entity EXP5EX2 is port (
13 |   A, B :in  std_logic_vector(3 DOWNTO 0);
14 |   S     :out std_logic_vector(4 DOWNTO 0));
15 end EXP5EX2;
16 -----
17
18 architecture ex1 of EXP5EX2 is
19
20 begin
21 |   S <= ('0' & unsigned(A)) + ('0' &  unsigned(B));
22 end ex1;
23
```

Arquivo tb_exp5ex2.vhd:

```
8  -----
9  LIBRARY ieee;
10 USE ieee.std_logic_1164.ALL;
11 USE std.textio.ALL;
12 USE ieee.numeric_std.ALL;
13 -----
14
15 ENTITY testbench_exp5ex2 IS END;
16
17 ARCHITECTURE tb_exp5ex2 OF testbench_exp5ex2 IS
18
19   component EXP5EX2
20
21   port (
22     A, B :in  std_logic_vector(3 DOWNTO 0);
23     S    :out std_logic_vector(4 DOWNTO 0));
24   end component;
25   -----
26
27   signal aa, bb : std_logic_vector (3 DOWNTO 0);
28
29   Begin
30
31   som: EXP5EX2 PORT MAP (A => aa, B => bb, S => open);
32
33   estimulo: PROCESS
34
35   begin
36     for i in 0 to 15 loop
37       aa <= std_logic_vector(to_unsigned(i, 4));
38       for j in 0 to 15 loop
39         bb <= std_logic_vector(to_unsigned(j, 4));
40         wait for 5 ns;
41       end loop;
42     end loop;
43   end PROCESS estimulo;
```

Compilação:




Name	Status	Type	Orig	Modified
exp5ex2.vhd	✓	VHDL	0	03/21/2021 11:21:26 am
tb_exp5ex2.vhd	✓	VHDL	1	03/21/2021 11:34:14 am

Project	sim
---------	-----

Transcript

```
# Compile of exp5ex2.vhd was successful.
# Compile of tb_exp5ex2.vhd was successful.
# 2 compiles, 0 failed with no errors.
```

Simulação:

   

	Entrada A	Entrada B	Saída S
Cursor 1	0000	1101	01101
Cursor 2	0001	1000	01001
Cursor 3	0010	0011	00101
Cursor 4	0111	1011	10010
Cursor 5	1000	1000	10000
Cursor 6	1001	0010	01011
Cursor 7	1110	0101	10011
Cursor 8	1111	1111	11110

Questão 3

Arquivo exp5ex3tm.vhd:

```
1  -- *****
2  -- Top Module para comparar as saídas dos
3  -- Circuitos:
4  -- 1. Somador de 4 palavras usando 4
5  -- somadores completos(Device Under Test);
6  -- 2. Somador de 4 palavras usando o operador
7  -- '+' da biblioteca std_logic_arith (Golden Model)
8  --
9  --
10 --      A,B   Vetores de Entrada
11 --      S_dut Saída do circuito 1
12 --      S_gm  Saída do circuito 2
13 -- *****
14 -----
15 library IEEE;
16 use IEEE.std_logic_1164.all;
17 use IEEE.std_logic_arith.all;
18 -----
19 entity EXP5EX3TM is
20 end EXP5EX3TM;
21 -----
22
23 architecture ex3 of EXP5EX3TM is
24
25     component EXP5_EX1 is port (
26         A, B :in  std_logic_vector(3 DOWNTO 0);
27         S    :out std_logic_vector(4 DOWNTO 0));
28     end component;
29
30     component EXP5EX2 is port (
31         A, B :in  std_logic_vector(3 DOWNTO 0);
32         S    :out std_logic_vector(4 DOWNTO 0));
33     end component;
34
35     component testbench_exp5ex3 is port (
36         S_dut, S_gm :in  STD_LOGIC_VECTOR(4 DOWNTO 0);
37         A, B        :out STD_LOGIC_VECTOR(3 DOWNTO 0));
38     end component;
39
40     signal A, B        : STD_LOGIC_VECTOR(3 DOWNTO 0);
41     signal S_dut, S_gm : STD_LOGIC_VECTOR(4 DOWNTO 0);
42
43     begin
44         U0: EXP5_EX1 PORT MAP(A, B, S_dut);
45         U1: EXP5EX2 PORT MAP(A, B, S_gm);
46         U2: TESTBENCH_EXP5EX3 PORT MAP(S_dut, S_gm, A, B);
47     end ex3;
```

Arquivo tb_exp5ex3.vhd:

```
14 -----
15 LIBRARY ieee;
16 USE ieee.std_logic_1164.ALL;
17 USE std.textio.ALL;
18 USE ieee.numeric_std.ALL;
19 -----
20
21 ENTITY testbench_exp5ex3 IS
22 port (S_dut, S_gm: in  STD_LOGIC_VECTOR(4 DOWNT0 0));
23       A, B           : out STD_LOGIC_VECTOR(3 DOWNT0 0));
24 END testbench_exp5ex3;
25
26
27 -----
28 ARCHITECTURE tb_exp5ex3 OF testbench_exp5ex3 IS
29
30 Begin
31
32
33 estimulo: PROCESS
34 begin
35     report "Iniciando teste..." severity NOTE;
36
37     for i in 0 to 15 loop
38         A <= std_logic_vector(to_unsigned(i, 4));
39         for j in 0 to 15 loop
40             B <= std_logic_vector(to_unsigned(j, 4));
41             wait for 500 ns;
42             assert (S_gm = S_dut) report "Falhou" severity ERROR;
43         end loop;
44     end loop;
45
46     report "Teste finalizado!" severity NOTE;
47
48     wait;
49
50 end PROCESS estimulo;
51
52 end tb_exp5ex3;
```

Compilação:


Name	Status	Type	Or	Modified
exp5_ex1.vhd	✓	VHDL	0	03/21/2021 12:37:23 am
exp5ex2.vhd	✓	VHDL	1	03/21/2021 04:04:22 pm
exp5ex3tm.vhd	✓	VHDL	2	03/21/2021 04:08:56 pm
tb_exp5ex3.vhd	✓	VHDL	3	03/21/2021 04:09:39 pm

Project	sim
---------	-----

Transcript

```
# Compile of exp5_ex1.vhd was successful.
# Compile of exp5ex2.vhd was successful.
# Compile of exp5ex3tm.vhd was successful.
# Compile of tb_exp5ex3.vhd was successful.
# 4 compiles, 0 failed with no errors.
```


Simulação:

 

	Entrada A	Entrada B	Saída S (DUT)	Saída S (GM)
Cursor 1	0010	1100	0111	0111
Cursor 2	0011	0110	0100	0100
Cursor 3	0100	0001	0010	0010
Cursor 4	1010	1101	1011	1011
Cursor 5	1011	0101	1000	1000
Cursor 6	1100	0010	0111	0111